

X PHYSICS SHORT NOTES

8. Current Electricity

A) CONCEPT OF CHARGE, CURRENT, POTENTIAL, POTENTIAL DIFFERENCE, AND RESISTANCE; OHM'S LAW

➤ Concept of charge:

- There are two kind of charges: Positive charge and Negative charge.
- Two like charges repel each other.
- Two unlike charge attract each other.
- The charge on one electron is -1.6×10^{-19} C.
- 1 C charge means a deficit of $\frac{1}{1.6 \times 10^{-19}} = 6.25 \times 10^{18}$ electrons.

➤ Concept of Current:

- **Definition:** Current is the rate of flow of charge.
- The current flowing in a conductor is the amount of charge flowing through it per second.
- $I = \frac{Q}{t} = \frac{ne}{t}$
- $Q = n \times e$
- The charge e on one electron is -1.6×10^{-19} coulomb.
- The current in a circuit is measured by an **ammeter** which is connected to the circuit in **series**.

➤ Concept of potential and potential difference (P.D.):

- **Definition:** The potential at a point is defined as the amount of work done per unit charge in bringing a unit **positive test charge from infinity** to a point.
- **Definition:** The potential difference between two points is defined as the amount of work done in bringing a **unit positive charge from one point** to the other.
- $V = \frac{W}{Q}$; where: V is the electric potential, W joule of work is done in bringing the test charge Q coulomb from infinity to the point P .
- Thus, $W = QV$; as the work is done to move a charge Q from infinity to a point P where electric potential is V .
- The potential difference between two points in an electric circuit is measured by a **voltmeter** which is connected in **parallel** with the circuit.

➤ **Concept of Resistance:**

- **Definition:** The obstruction offered to the flow of current by the wire or a conductor is called its resistance.
- Its unit is ohm or Ω

➤ **Conductance:**

- **Definition:** The reciprocal of resistance is called conductance.
- Conductance = $\frac{1}{\text{Resistance}}$.
- Its unit is $(\text{ohm})^{-1}$ or siemen or Ω^{-1} .

➤ **Ohm's Law (V = IR):**


- **Definition:** According to Ohm's law, the current flowing in a conductor is directly proportional to the potential difference applied across its ends provided that the physical conditions (like temperature) remains constant.
- If the **potential difference** across the ends of a conductor is **doubled**, the **current** flowing in it also gets **doubled**.

➤ **Graphs:**

○ **I-V graph - Conductance:**

▪ **Slope of I-V graph:**

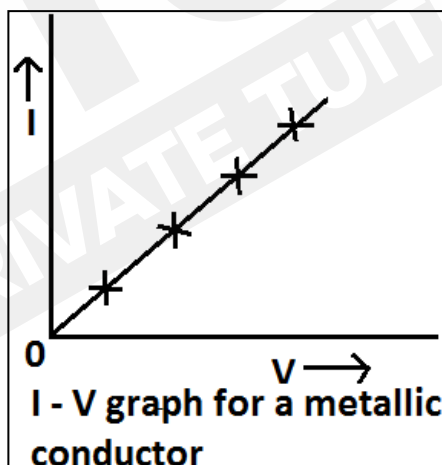- Slope of I-V graph = $\frac{\Delta I}{\Delta V} = \frac{1}{\text{Resistance of the conductor}}$
- It gives conductance.




○ **V-I graph- Resistance:**

▪ **Slope of V-I graph:**

- The slope of V-I graph = $\frac{\Delta V}{\Delta I} = R$
- It gives the resistance R of the conductor.

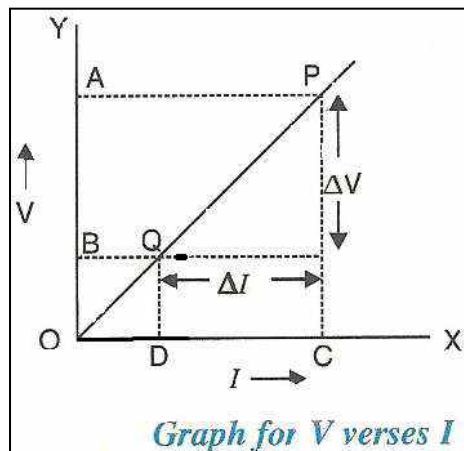- **Steeper the slope of V-I graph, greater is the resistance of conductor.**



➤ **Distinction between the ohmic and non-ohmic resistors:**

Ohmic resistor	Non-ohmic resistor
1. It obeys the Ohm's law; V/I is constant for all values of V or I .	1. It does not obey the Ohm's law; V/I is different for all values of V or I .
2. The V/I graph is a straight line from origin.	2. The V/I graph is a curve, which may not pass through the origin
3. The slope of $V-I$ graph is same for all values of V or I at a given temperature.	3. The slope of $V-I$ graph is different for all values of V or I even at a given temperature.
4. Examples: All metallic conductors such as nichrome, silver, copper, electrolytes with suitable electrodes etc.	4. Examples: filament of a bulb, Junction diode, LED, transistor, etc.

➤ **Factors affecting resistance:**

- Factors affecting the resistance of a conductor are:
 - Nature/Material of the conductor:
 - The resistance is **less** for a **good** conductor.
 - The resistance is **large** for a **bad** conductor (or insulator).
 - Length of the conductor – **Directly Proportional**
 - Thickness of the conductor – **Inversely Proportional.**
 - Temperature of the conductor – **Directly Proportional.**

➤ **Specific Resistance or Resistivity:**

- **Definition:** Specific resistance of a material is the resistance of the wire of particular material having unit length and unit area of cross section.
- \therefore Resistivity $\rho = \frac{Ra}{l}$.

➤ **Conductivity:**

- **Definition:** The reciprocal of resistivity is called the **conductivity**.
- It is represented by the symbol σ (sigma).
- $\sigma = \frac{1}{\rho} = \frac{l}{Ra}$

➤ **Superconductor:**

- **Definition:** A superconductor is a substance of zero resistance at very low temperature.
- Examples of super conductors:
 - Mercury at 4.2 K.
 - Niobium below 9.2 K.
 - Lead below 7.25 K.
- **Superconductivity:** The property of having zero resistance at a low temperature is called **superconductivity**.

➤ **FORMULAE:**

1. $V = IR$

2. $I = \frac{V}{R}$

3. $R = \frac{V}{I}$

4. $R = \rho \frac{l}{a} = \rho \frac{l}{\pi r^2}$

5. $\rho = \frac{Ra}{l} = \frac{R \pi r^2}{l}$

6. $I = \frac{Q}{t} = \frac{ne}{t}$

7. $W = QV$

8. $V = IR$ (external)

9. $V = Ir$ (internal)

B) ELECTRO-MOTIVE FORCE, TERMINAL VOLTAGE & INTERNAL RESISTANCE OF CELL; COMBINATION OF RESISTORS.

➤ Electro-motive force (e.m.f.):

- **Definition of Electromotive force:** The e.m.f. of a cell is the work done or energy spent per unit charge in taking a unit positive charge around the complete circuit (outside and inside) of the cell.
- $\mathcal{E} = w/Q$
- S.I. unit is volt (V).
- **Terminal Voltage:**
 - **Definition:** The work done per unit charge in carrying a unit positive test charge around the circuit connected across the terminals (outside) of the cell is termed as the **terminal voltage** of a cell.
 - S.I. unit is volt (V).
- **Voltage drop in a cell:**
 - **Definition:** The **voltage drop** in the cell is the work done in carrying a unit positive charge through the electrolyte.
- **Internal resistance of a cell:**
 - **Definition:** Internal resistance of cell is the resistance offered by the electrolyte inside the cell, to the flow of current in the cell.
 - It is denoted by symbol r .
 - Its unit is ohm Ω .

➤ Combination of resistors:

- **Expression for equivalent resistance in series:**
 - $R_s = R_1 + R_2 + R_3$
 - $R_s = R_1 + R_2 + R_3 + \dots + R_n$; where n is number of resistances.
 - $R_s = nR$; if n is number of **equal** resistances.
- **Expression for the equivalent resistance in parallel:**
 - $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$
 - $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$; where n is the no. of resistors.
 - $R_p = \frac{R}{n}$; where n is number of **equal** resistances.

➤ **FORMULAE:**

1. $V = IR$
2. Resistivity $\rho = \frac{Ra}{l}$
3. Total resistance of the circuit $= R + r$
4. Current drawn from the cell $I = \frac{E}{R+r}$
5. Terminal voltage of the cell $V = IR = \frac{ER}{R+r}$
6. Voltage drop inside the cell $v = Ir = \frac{Er}{R+r}$
7. E.m.f of cell, $E = I(R+r)$
8. Internal resistance of the cell, $r = \left(\frac{E}{V} - 1\right) R$
9. Equivalent resistance in series $R_s = R + R + R \dots$
10. Equivalent resistance in parallel $\frac{1}{R_p} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R} \dots$
11. $I = \frac{Q}{t} = \frac{ne}{t}$
12. Charge of 1 electron $= -1.6 \times 10^{-19} \text{ C}$
13. 1 A current carries 6.25×10^{18} elec.

C) ELECTRICAL ENERGY AND POWER

➤ **Electrical energy:**

- Energy exists in various forms such as mechanical, heat, chemical, electrical, light, nuclear, etc.
- **According to the law of conservation of energy:** Energy can be transformed from one form to another, but it can neither be created nor destroyed.
- **Measurement of electrical energy (expression $W = QV = VIt$):**
 - Electrical energy supplied by the source is :

$$W = QV \text{ joule} = VIt \text{ joule} = I^2Rt \text{ joule} = \frac{V^2 t}{R} \text{ joule.}$$
 - S.I. unit of electrical energy is joule (J).

➤ **Electrical power: $[P = \frac{W}{t} = VI]$.**

- **Definition of Power:** Power is the rate of doing work.
- **Definition of electrical power:** Rate at which electrical energy is supplied by the source.
- $Power = \frac{\text{Energy supplied}}{\text{Time}}$
- Electrical power is: $P = \frac{W}{t} \text{ watt} = \frac{QV}{t} \text{ watt} = VI \text{ watt} = I^2R \text{ watt} = \frac{V^2}{R} \text{ watt.}$

➤ **Commercial units of electrical energy:**

- watt × hour (Wh)
- kilo-watt hour (kWh).
- **Power rating of some common appliances:**

Appliance	Power (in watt)	Voltage (in volt)
Car bulb	20	12
Electric bulb	15-200	220
Room heater	1000	220
Electric iron	700	220
Electric mixer	750	220
Geyser	1500	220
Electric kettle	2000	220

In our country, a.c. is supply voltage = 220V.

➤ **Household consumption of electrical energy:**

- Electrical Energy (kWh) = $\frac{\text{Power (watt)} \times \text{Time (hour)}}{1000}$
 $= \frac{V \text{ (volt)} \times I \text{ (ampere)} \times t \text{ (hour)}}{1000}$
- The cost of electricity = electrical energy (kWh) × rate per kWh.
- **Example:**
 - If an electric oven of power 5kW is used for 2h each day.
 - The electrical energy consumed per day = 10kWh.
 - Energy consumed in the whole month is 10 × 30 = 300kWh.
 - Rate of electrical energy = Rs. 3.00.
 - ∴ The cost = 300 × 3.00 = Rs. 900.

➤ **Heating effect of current:**

- **Joule's law of heating:** It is the relation obtained to show the amount of heat produced is directly proportional to square of current, resistance and time.
- Thus Joule's law of heating, $H \propto I^2 R t$ joule or $H = 0.24 I^2 R t$ cal.

➤ **FORMULAE:**

$$1. \quad W = QV = V I t = I^2 R t = \frac{V^2 T}{R} = P \times t$$

$$2. \quad P = \frac{W}{t} = V I = I^2 R = \frac{V^2}{R}$$

